


Some Applications of 2-D Systems of Differential Equations

Xu-Yan Chen

Examples:

- ▶ Salt in Tanks (a linear system)
- ▶ Electric Circuits (a linear system)
- ▶ Population Model - Competing Species (a nonlinear system)

Example 2. (Electric Circuit)

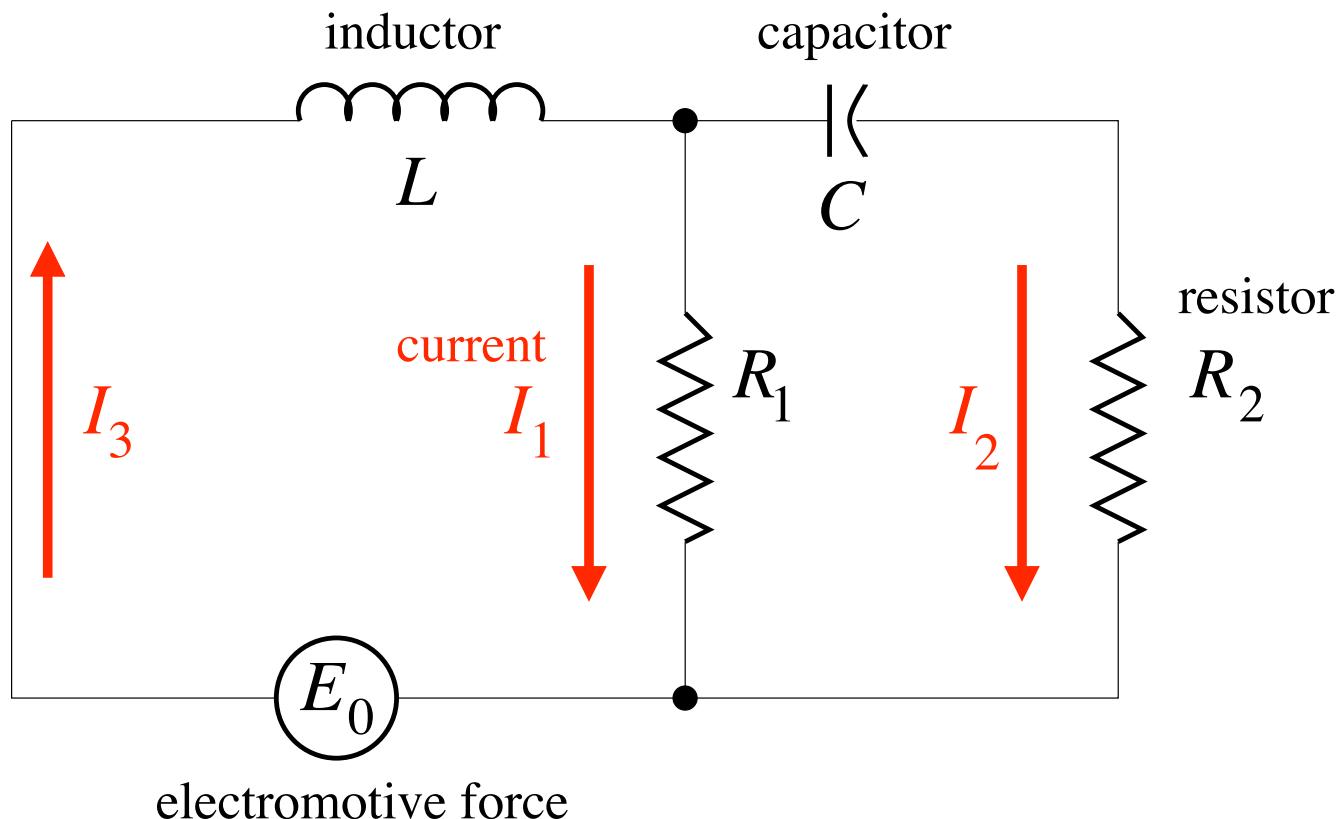


Question: Given $\begin{cases} R_1 = 50 \text{ ohms}, & R_2 = 25 \text{ ohms}, \\ L = 2 \text{ henries}, & C = 0.008 \text{ farads}, \\ E_0 = 100 \text{ volts}, \end{cases}$

and the initial condition $I_1(0) = I_2(0) = I_3(0) = 0$ amps,
find electric currents $I_1(t), I_2(t), I_3(t)$.

Example 2. (continued. Review of Physics.)

Definition of Current:


$$I = \frac{dQ}{dt} \quad \left(\begin{array}{l} \text{the rate of change} \\ \text{of charge } Q \end{array} \right)$$

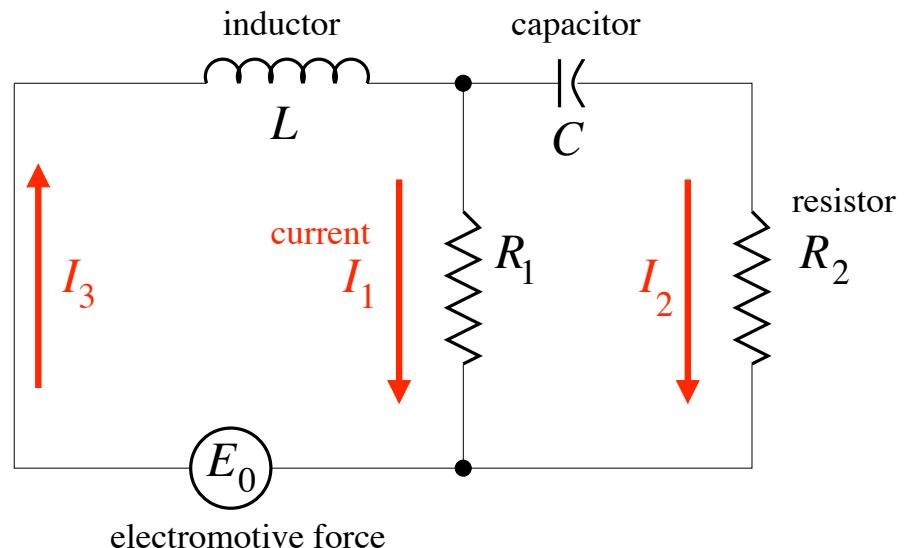

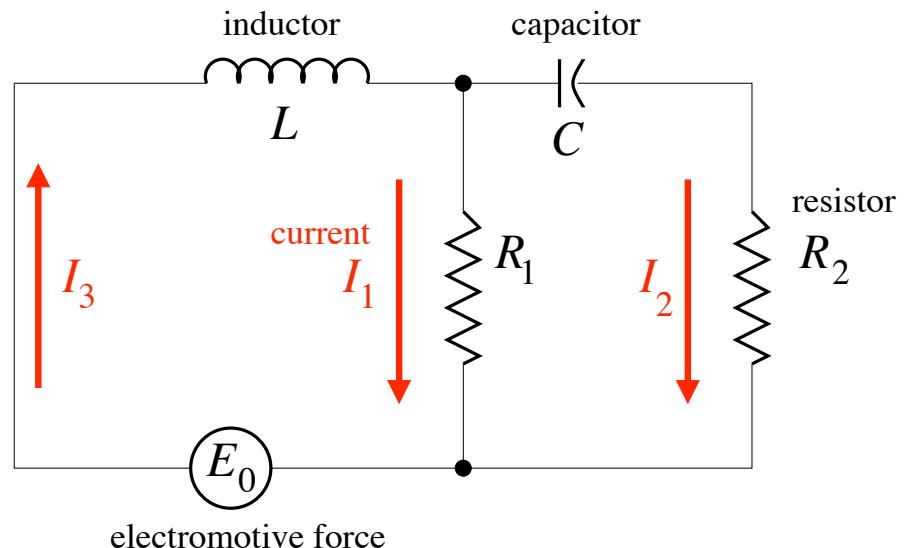Example 2. (continued. Review of Physics.)

Definition of Current:

$$I = \frac{dQ}{dt} \quad \left(\begin{array}{l} \text{the rate of change} \\ \text{of charge } Q \end{array} \right)$$




| Circuit Element | inductor | resistor | capacitor |
|-----------------|------------------------------|----------------------|--------------------------|
| Voltage Drop | $L dI/dt$ (Faraday's law) | $R I$ (Ohm's law) | Q/C (Coulomb's law) |

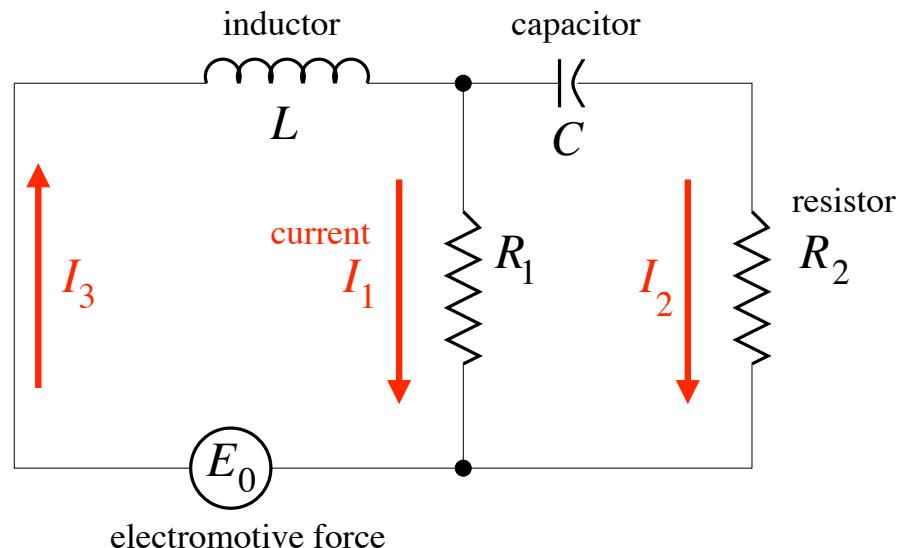Example 2. (continued. Review of Physics.)

Definition of Current:

$$I = \frac{dQ}{dt} \quad \left(\begin{array}{l} \text{the rate of change} \\ \text{of charge } Q \end{array} \right)$$




| Circuit Element | inductor | resistor | capacitor |
|-----------------|------------------------------|----------------------|--------------------------|
| Voltage Drop | $L dI/dt$ (Faraday's law) | $R I$ (Ohm's law) | Q/C (Coulomb's law) |

Kirchhoff's Current Law: $I_1 + I_2 = I_3$

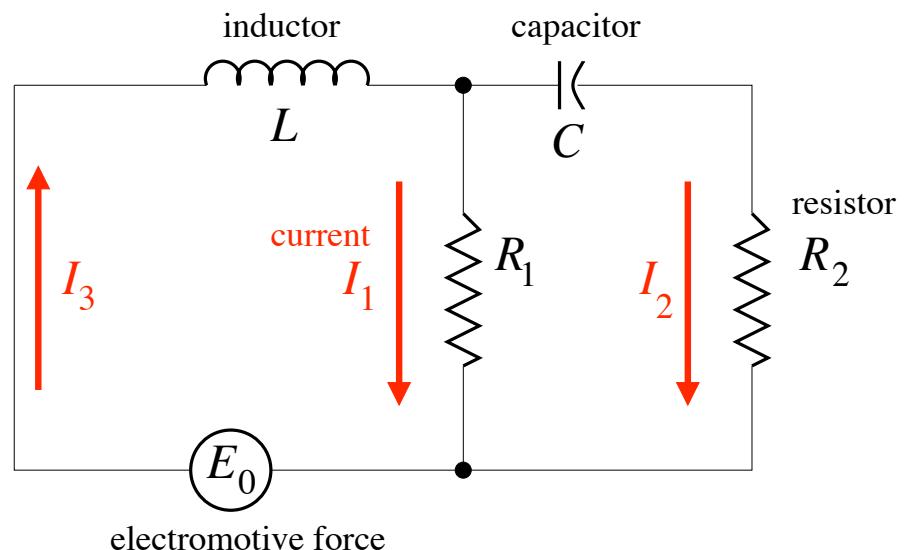Example 2. (continued. Review of Physics.)

Definition of Current:

$$I = \frac{dQ}{dt} \quad (\text{the rate of change of charge } Q)$$



| Circuit Element | inductor | resistor | capacitor |
|-----------------|------------------------------|----------------------|--------------------------|
| Voltage Drop | $L dI/dt$ (Faraday's law) | $R I$ (Ohm's law) | Q/C (Coulomb's law) |

Kirchhoff's Current Law: $I_1 + I_2 = I_3$


Kirchhoff's Voltage Law:

(the sum of voltage drops in a closed loop) = 0

Example 2. (continued. Apply Kirchhoff's law.)

$$I = dQ/dt$$

$$I_1 + I_2 = I_3$$

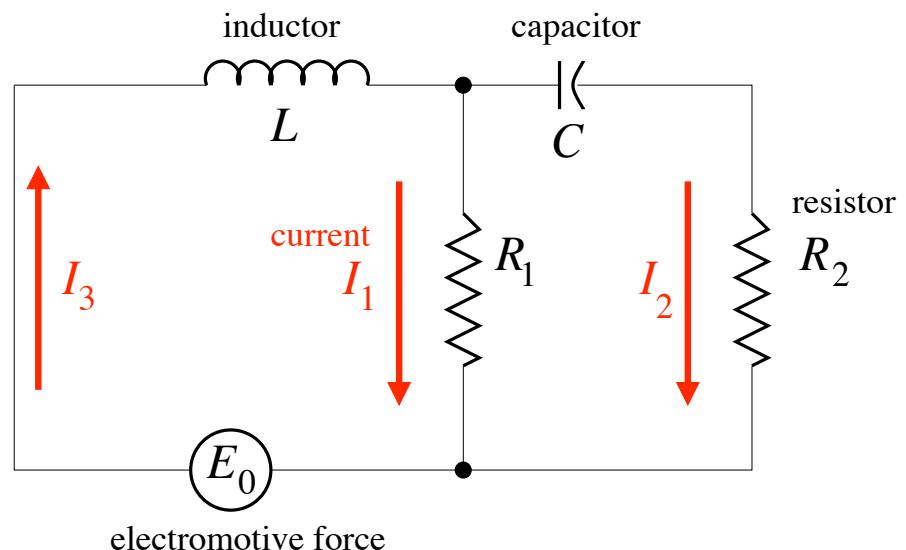

| Circuit Element | inductor | resistor | capacitor |
|-----------------|-----------|----------|-----------|
| Voltage Drop | $L dI/dt$ | $R I$ | Q/C |


Kirchhoff's Voltage Law

(the sum of voltage drops in a closed loop) = 0

Example 2. (continued. Apply Kirchhoff's law.)

$$I = dQ/dt$$

$$I_1 + I_2 = I_3$$

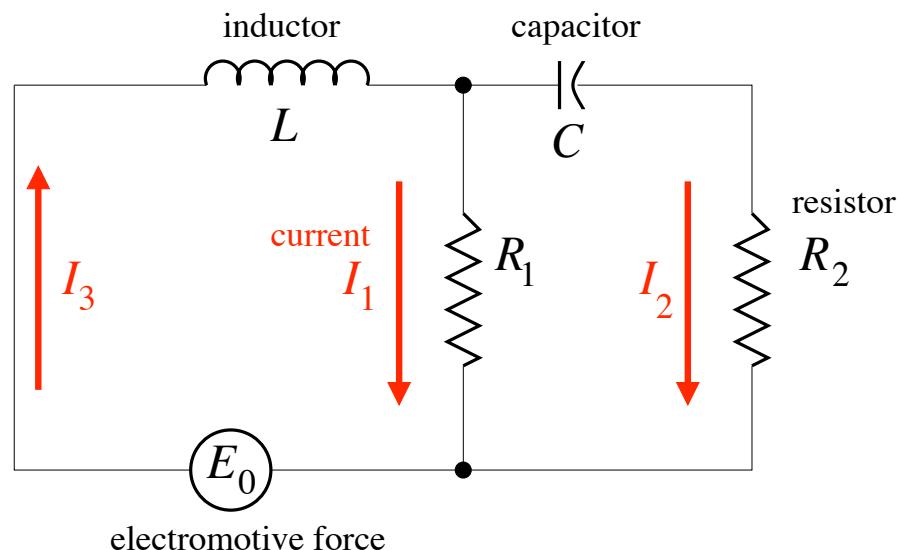

| Circuit Element | inductor | resistor | capacitor |
|-----------------|-----------|----------|-----------|
| Voltage Drop | $L dI/dt$ | $R I$ | Q/C |

Kirchhoff's Voltage Law

(the sum of voltage drops in a closed loop) = 0


The Left Loop

$$L \frac{dI_3}{dt} + R_1 I_1 - E_0 = 0$$

Example 2. (continued. Apply Kirchhoff's law.)

$$I = dQ/dt$$

$$I_1 + I_2 = I_3$$

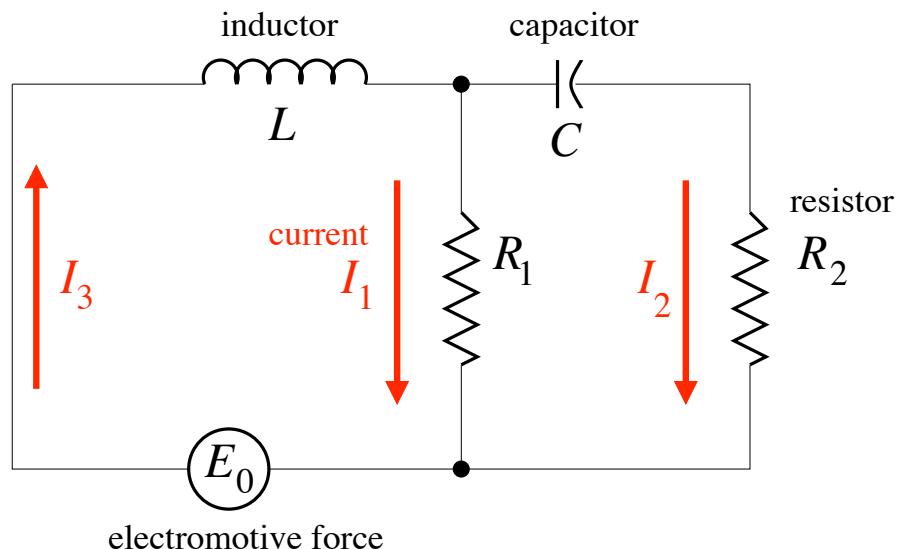

| Circuit Element | inductor | resistor | capacitor |
|-----------------|-----------|----------|-----------|
| Voltage Drop | $L dI/dt$ | $R I$ | Q/C |

Kirchhoff's Voltage Law

(the sum of voltage drops in a closed loop) = 0

The Left Loop

$$L \frac{dI_3}{dt} + R_1 I_1 - E_0 = 0$$


The Right Loop

$$\frac{1}{C} Q_2 + R_2 I_2 - R_1 I_1 = 0$$

Example 2. (continued. Set up equations.)

$$I = dQ/dt$$

$$I_1 + I_2 = I_3$$

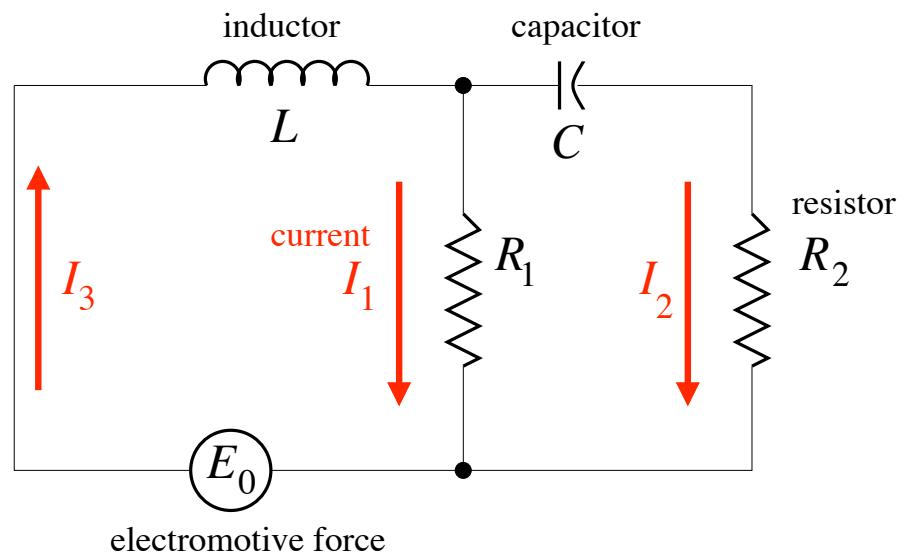

The Left Loop

$$L \frac{dI_3}{dt} + R_1 I_1 - E_0 = 0$$


The Right Loop

$$\frac{1}{C} Q_2 - R_1 I_1 + R_2 I_2 = 0$$

Example 2. (continued. Set up equations.)

$$I = dQ/dt$$

$$I_1 + I_2 = I_3$$

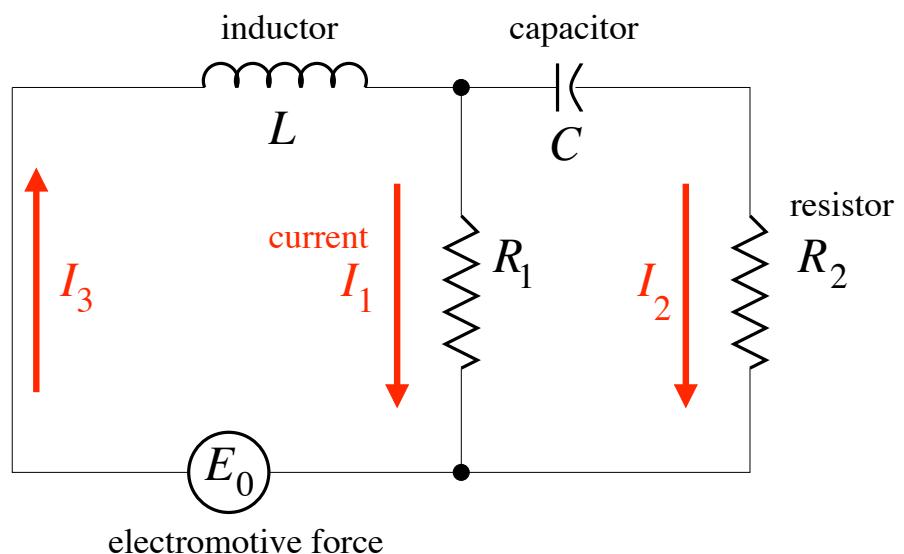

The Left Loop

$$L \frac{dI_3}{dt} + R_1 I_1 - E_0 = 0$$

$$\Downarrow \quad I_3 = I_1 + I_2$$

$$L \frac{dI_1}{dt} + L \frac{dI_2}{dt} + R_1 I_1 - E_0 = 0$$


The Right Loop

$$\frac{1}{C} Q_2 - R_1 I_1 + R_2 I_2 = 0$$

Example 2. (continued. Set up equations.)

$$I = dQ/dt$$

$$I_1 + I_2 = I_3$$

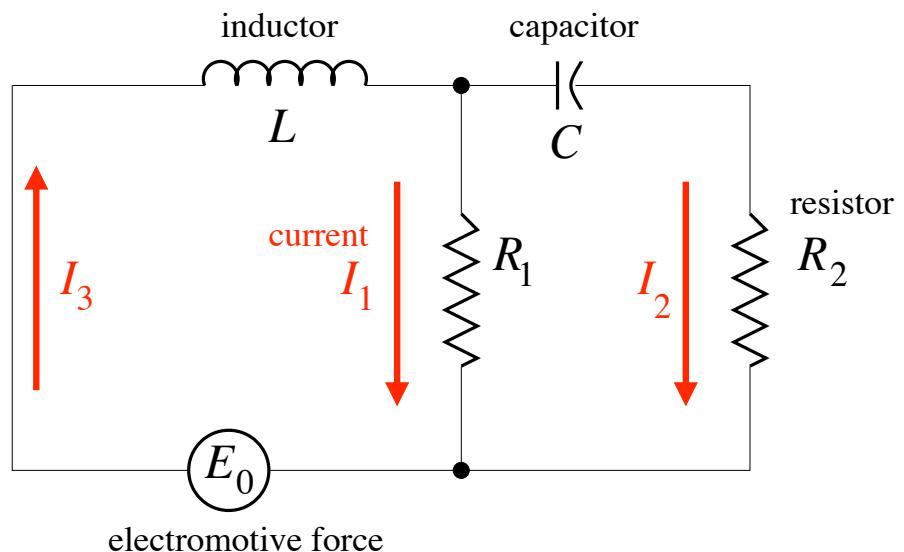

The Left Loop

$$L \frac{dI_3}{dt} + R_1 I_1 - E_0 = 0$$

$$\Downarrow I_3 = I_1 + I_2$$

$$L \frac{dI_1}{dt} + L \frac{dI_2}{dt} + R_1 I_1 - E_0 = 0$$

The Right Loop

$$\frac{1}{C} Q_2 - R_1 I_1 + R_2 I_2 = 0$$

$$\Downarrow \frac{d}{dt}$$

$$\frac{1}{C} I_2 - R_1 \frac{dI_1}{dt} + R_2 \frac{dI_2}{dt} = 0$$

Example 2. (continued. Set up equations.)

$$\begin{cases} LI'_1 + LI'_2 + R_1 I_1 - E_0 = 0 \\ \frac{1}{C} I_2 - R_1 I'_1 + R_2 I'_2 = 0 \end{cases}$$

Example 2. (continued. Set up equations.)

$$\begin{cases} LI'_1 + LI'_2 + R_1 I_1 - E_0 = 0 \\ \frac{1}{C} I_2 - R_1 I'_1 + R_2 I'_2 = 0 \end{cases}$$

$$\begin{cases} LI'_1 + LI'_2 = -R_1 I_1 + E_0 \\ -R_1 I'_1 + R_2 I'_2 = -\frac{1}{C} I_2 \end{cases}$$

Example 2. (continued. Set up equations.)

$$\begin{cases} LI'_1 + LI'_2 + R_1 I_1 - E_0 = 0 \\ \frac{1}{C} I_2 - R_1 I'_1 + R_2 I'_2 = 0 \end{cases} \quad \begin{cases} LI'_1 + LI'_2 = -R_1 I_1 + E_0 \\ -R_1 I'_1 + R_2 I'_2 = -\frac{1}{C} I_2 \end{cases}$$

Equilibrium: $\begin{cases} 0 = -R_1 I_1 + E_0 \\ 0 = -\frac{1}{C} I_2 \end{cases} \Rightarrow \begin{cases} I_1 = E_0 / R_1 \\ I_2 = 0 \end{cases}$

Example 2. (continued. Set up equations.)

$$\begin{cases} LI'_1 + LI'_2 + R_1 I_1 - E_0 = 0 \\ \frac{1}{C} I_2 - R_1 I'_1 + R_2 I'_2 = 0 \end{cases} \quad \begin{cases} LI'_1 + LI'_2 = -R_1 I_1 + E_0 \\ -R_1 I'_1 + R_2 I'_2 = -\frac{1}{C} I_2 \end{cases}$$

Equilibrium: $\begin{cases} 0 = -R_1 I_1 + E_0 \\ 0 = -\frac{1}{C} I_2 \end{cases} \Rightarrow \begin{cases} I_1 = E_0 / R_1 \\ I_2 = 0 \end{cases}$

Time-Dependent Equations in Matrix Form:

$$\begin{bmatrix} L & L \\ -R_1 & R_2 \end{bmatrix} \begin{bmatrix} I'_1 \\ I'_2 \end{bmatrix} = \begin{bmatrix} -R_1 & 0 \\ 0 & -\frac{1}{C} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} + \begin{bmatrix} E_0 \\ 0 \end{bmatrix}$$

Example 2. (continued. Set up equations.)

$$\begin{cases} LI'_1 + LI'_2 + R_1 I_1 - E_0 = 0 \\ \frac{1}{C} I_2 - R_1 I'_1 + R_2 I'_2 = 0 \end{cases} \quad \begin{cases} LI'_1 + LI'_2 = -R_1 I_1 + E_0 \\ -R_1 I'_1 + R_2 I'_2 = -\frac{1}{C} I_2 \end{cases}$$

Equilibrium: $\begin{cases} 0 = -R_1 I_1 + E_0 \\ 0 = -\frac{1}{C} I_2 \end{cases} \Rightarrow \begin{cases} I_1 = E_0 / R_1 \\ I_2 = 0 \end{cases}$

Time-Dependent Equations in Matrix Form:

$$\begin{bmatrix} L & L \\ -R_1 & R_2 \end{bmatrix} \begin{bmatrix} I'_1 \\ I'_2 \end{bmatrix} = \begin{bmatrix} -R_1 & 0 \\ 0 & -\frac{1}{C} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} + \begin{bmatrix} E_0 \\ 0 \end{bmatrix}$$

$$\begin{bmatrix} I'_1 \\ I'_2 \end{bmatrix} = \begin{bmatrix} L & L \\ -R_1 & R_2 \end{bmatrix}^{-1} \begin{bmatrix} -R_1 & 0 \\ 0 & -\frac{1}{C} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} + \begin{bmatrix} L & L \\ -R_1 & R_2 \end{bmatrix}^{-1} \begin{bmatrix} E_0 \\ 0 \end{bmatrix}$$

Example 2. (continued. Set up equations.)

$$\begin{cases} LI'_1 + LI'_2 + R_1 I_1 - E_0 = 0 \\ \frac{1}{C} I_2 - R_1 I'_1 + R_2 I'_2 = 0 \end{cases} \quad \begin{cases} LI'_1 + LI'_2 = -R_1 I_1 + E_0 \\ -R_1 I'_1 + R_2 I'_2 = -\frac{1}{C} I_2 \end{cases}$$

Equilibrium: $\begin{cases} 0 = -R_1 I_1 + E_0 \\ 0 = -\frac{1}{C} I_2 \end{cases} \Rightarrow \begin{cases} I_1 = E_0/R_1 \\ I_2 = 0 \end{cases}$

Time-Dependent Equations in Matrix Form:

$$\begin{bmatrix} L & L \\ -R_1 & R_2 \end{bmatrix} \begin{bmatrix} I'_1 \\ I'_2 \end{bmatrix} = \begin{bmatrix} -R_1 & 0 \\ 0 & -\frac{1}{C} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} + \begin{bmatrix} E_0 \\ 0 \end{bmatrix}$$

$$\begin{bmatrix} I'_1 \\ I'_2 \end{bmatrix} = \begin{bmatrix} L & L \\ -R_1 & R_2 \end{bmatrix}^{-1} \begin{bmatrix} -R_1 & 0 \\ 0 & -\frac{1}{C} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} + \begin{bmatrix} L & L \\ -R_1 & R_2 \end{bmatrix}^{-1} \begin{bmatrix} E_0 \\ 0 \end{bmatrix}$$

2-D System:
$$\begin{bmatrix} I'_1 \\ I'_2 \end{bmatrix} = \begin{bmatrix} -\frac{R_1 R_2}{L(R_1+R_2)} & \frac{1}{C(R_1+R_2)} \\ -\frac{R_1^2}{L(R_1+R_2)} & \frac{1}{C(R_1+R_2)} \end{bmatrix} \begin{bmatrix} I_1 - \frac{E_0}{R_1} \\ I_2 \end{bmatrix}$$

Example 2. (continued. Plug in numbers.)

2-D System:
$$\begin{bmatrix} I'_1 \\ I'_2 \end{bmatrix} = \begin{bmatrix} -\frac{R_1 R_2}{L(R_1+R_2)} & \frac{1}{C(R_1+R_2)} \\ -\frac{R_1^2}{L(R_1+R_2)} & -\frac{1}{C(R_1+R_2)} \end{bmatrix} \begin{bmatrix} I_1 - \frac{E_0}{R_1} \\ I_2 \end{bmatrix}$$

Plug in $\left\{ \begin{array}{ll} R_1 = 50 \text{ ohms}, & R_2 = 25 \text{ ohms}, \\ L = 2 \text{ henries}, & C = 0.008 \text{ farads}, \quad E_0 = 100 \text{ volts}, \end{array} \right.$

Example 2. (continued. Plug in numbers.)

2-D System:
$$\begin{bmatrix} I'_1 \\ I'_2 \end{bmatrix} = \begin{bmatrix} -\frac{R_1 R_2}{L(R_1+R_2)} & \frac{1}{C(R_1+R_2)} \\ -\frac{R_1^2}{L(R_1+R_2)} & -\frac{1}{C(R_1+R_2)} \end{bmatrix} \begin{bmatrix} I_1 - \frac{E_0}{R_1} \\ I_2 \end{bmatrix}$$

Plug in $\begin{cases} R_1 = 50 \text{ ohms}, & R_2 = 25 \text{ ohms}, \\ L = 2 \text{ henries}, & C = 0.008 \text{ farads}, \quad E_0 = 100 \text{ volts}, \end{cases}$

2-D System:
$$\begin{bmatrix} I'_1 \\ I'_2 \end{bmatrix} = \begin{bmatrix} -25/3 & 5/3 \\ -50/3 & -5/3 \end{bmatrix} \begin{bmatrix} I_1 - 2 \\ I_2 \end{bmatrix}$$

Example 2. (continued. Solve the system.)

Initial Value Problem

$$\begin{bmatrix} I'_1 \\ I'_2 \end{bmatrix} = \begin{bmatrix} -25/3 & 5/3 \\ -50/3 & -5/3 \end{bmatrix} \begin{bmatrix} I_1 - 2 \\ I_2 \end{bmatrix}, \quad \begin{bmatrix} I_1(0) \\ I_2(0) \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \end{bmatrix}.$$

Example 2. (continued. Solve the system.)

Initial Value Problem

$$\begin{bmatrix} I'_1 \\ I'_2 \end{bmatrix} = \begin{bmatrix} -25/3 & 5/3 \\ -50/3 & -5/3 \end{bmatrix} \begin{bmatrix} I_1 - 2 \\ I_2 \end{bmatrix}, \quad \begin{bmatrix} I_1(0) \\ I_2(0) \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \end{bmatrix}.$$

Eigenvalues: $\lambda_1 = -5 + \frac{5}{3}\sqrt{6}i$, $\lambda_2 = -5 - \frac{5}{3}\sqrt{6}i$ (complex)

An Eigenvector for λ_1 : $\vec{w}_1 = \begin{bmatrix} 1 \\ 2 + \sqrt{6}i \end{bmatrix} = \begin{bmatrix} 1 \\ 2 \end{bmatrix} + i \begin{bmatrix} 0 \\ \sqrt{6} \end{bmatrix}$

Example 2. (continued. Solve the system.)

Initial Value Problem

$$\begin{bmatrix} I'_1 \\ I'_2 \end{bmatrix} = \begin{bmatrix} -25/3 & 5/3 \\ -50/3 & -5/3 \end{bmatrix} \begin{bmatrix} I_1 - 2 \\ I_2 \end{bmatrix}, \quad \begin{bmatrix} I_1(0) \\ I_2(0) \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \end{bmatrix}.$$

Eigenvalues: $\lambda_1 = -5 + \frac{5}{3}\sqrt{6}i$, $\lambda_2 = -5 - \frac{5}{3}\sqrt{6}i$ (complex)

An Eigenvector for λ_1 : $\vec{w}_1 = \begin{bmatrix} 1 \\ 2 + \sqrt{6}i \end{bmatrix} = \begin{bmatrix} 1 \\ 2 \end{bmatrix} + i \begin{bmatrix} 0 \\ \sqrt{6} \end{bmatrix}$

General solutions:

$$\begin{bmatrix} I_1(t) \\ I_2(t) \end{bmatrix} = \begin{bmatrix} 2 \\ 0 \end{bmatrix} + C_1 e^{-5t} \left\{ \cos\left(\frac{5\sqrt{6}}{3}t\right) \begin{bmatrix} 1 \\ 2 \end{bmatrix} - \sin\left(\frac{5\sqrt{6}}{3}t\right) \begin{bmatrix} 0 \\ \sqrt{6} \end{bmatrix} \right\} + C_2 e^{-5t} \left\{ \sin\left(\frac{5\sqrt{6}}{3}t\right) \begin{bmatrix} 1 \\ 2 \end{bmatrix} + \cos\left(\frac{5\sqrt{6}}{3}t\right) \begin{bmatrix} 0 \\ \sqrt{6} \end{bmatrix} \right\}$$

Example 2. (continued. Initial Condition.)

General solutions:

$$\begin{bmatrix} I_1(t) \\ I_2(t) \end{bmatrix} = \begin{bmatrix} 2 \\ 0 \end{bmatrix} + C_1 e^{-5t} \left\{ \cos\left(\frac{5\sqrt{6}}{3}t\right) \begin{bmatrix} 1 \\ 2 \end{bmatrix} - \sin\left(\frac{5\sqrt{6}}{3}t\right) \begin{bmatrix} 0 \\ \sqrt{6} \end{bmatrix} \right\} \\ + C_2 e^{-5t} \left\{ \sin\left(\frac{5\sqrt{6}}{3}t\right) \begin{bmatrix} 1 \\ 2 \end{bmatrix} + \cos\left(\frac{5\sqrt{6}}{3}t\right) \begin{bmatrix} 0 \\ \sqrt{6} \end{bmatrix} \right\}$$

Example 2. (continued. Initial Condition.)

General solutions:

$$\begin{bmatrix} I_1(t) \\ I_2(t) \end{bmatrix} = \begin{bmatrix} 2 \\ 0 \end{bmatrix} + C_1 e^{-5t} \left\{ \cos\left(\frac{5\sqrt{6}}{3}t\right) \begin{bmatrix} 1 \\ 2 \end{bmatrix} - \sin\left(\frac{5\sqrt{6}}{3}t\right) \begin{bmatrix} 0 \\ \sqrt{6} \end{bmatrix} \right\}$$
$$+ C_2 e^{-5t} \left\{ \sin\left(\frac{5\sqrt{6}}{3}t\right) \begin{bmatrix} 1 \\ 2 \end{bmatrix} + \cos\left(\frac{5\sqrt{6}}{3}t\right) \begin{bmatrix} 0 \\ \sqrt{6} \end{bmatrix} \right\}$$

Initial Condition:

$$\begin{bmatrix} I_1(0) \\ I_2(0) \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \end{bmatrix} \xrightarrow{\textcolor{red}{\Rightarrow}} \begin{bmatrix} 0 \\ 0 \end{bmatrix} = \begin{bmatrix} 2 \\ 0 \end{bmatrix} + C_1 \begin{bmatrix} 1 \\ 2 \end{bmatrix} + C_2 \begin{bmatrix} 0 \\ \sqrt{6} \end{bmatrix} \xrightarrow{\textcolor{red}{\Rightarrow}} \begin{bmatrix} C_1 \\ C_2 \end{bmatrix} = \begin{bmatrix} -2 \\ \frac{2}{3}\sqrt{6} \end{bmatrix}$$

Example 2. (continued. Initial Condition.)

General solutions:

$$\begin{bmatrix} I_1(t) \\ I_2(t) \end{bmatrix} = \begin{bmatrix} 2 \\ 0 \end{bmatrix} + C_1 e^{-5t} \left\{ \cos\left(\frac{5\sqrt{6}}{3}t\right) \begin{bmatrix} 1 \\ 2 \end{bmatrix} - \sin\left(\frac{5\sqrt{6}}{3}t\right) \begin{bmatrix} 0 \\ \sqrt{6} \end{bmatrix} \right\} \\ + C_2 e^{-5t} \left\{ \sin\left(\frac{5\sqrt{6}}{3}t\right) \begin{bmatrix} 1 \\ 2 \end{bmatrix} + \cos\left(\frac{5\sqrt{6}}{3}t\right) \begin{bmatrix} 0 \\ \sqrt{6} \end{bmatrix} \right\}$$

Initial Condition:

$$\begin{bmatrix} I_1(0) \\ I_2(0) \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \end{bmatrix} \xrightarrow{\textcolor{red}{\Rightarrow}} \begin{bmatrix} 0 \\ 0 \end{bmatrix} = \begin{bmatrix} 2 \\ 0 \end{bmatrix} + C_1 \begin{bmatrix} 1 \\ 2 \end{bmatrix} + C_2 \begin{bmatrix} 0 \\ \sqrt{6} \end{bmatrix} \xrightarrow{\textcolor{red}{\Rightarrow}} \begin{bmatrix} C_1 \\ C_2 \end{bmatrix} = \begin{bmatrix} -2 \\ \frac{2}{3}\sqrt{6} \end{bmatrix}$$

Solution of the initial value problem:

$$\begin{aligned} I_1(t) &= 2 - 2e^{-5t} \cos\left(\frac{5\sqrt{6}}{3}t\right) + \frac{2}{3}\sqrt{6}e^{-5t} \sin\left(\frac{5\sqrt{6}}{3}t\right) \\ I_2(t) &= \frac{10}{3}\sqrt{6}e^{-5t} \sin\left(\frac{5\sqrt{6}}{3}t\right) \end{aligned}$$

Example 2. (continued. Initial Condition.)

General solutions:

$$\begin{bmatrix} I_1(t) \\ I_2(t) \end{bmatrix} = \begin{bmatrix} 2 \\ 0 \end{bmatrix} + C_1 e^{-5t} \left\{ \cos\left(\frac{5\sqrt{6}}{3}t\right) \begin{bmatrix} 1 \\ 2 \end{bmatrix} - \sin\left(\frac{5\sqrt{6}}{3}t\right) \begin{bmatrix} 0 \\ \sqrt{6} \end{bmatrix} \right\} \\ + C_2 e^{-5t} \left\{ \sin\left(\frac{5\sqrt{6}}{3}t\right) \begin{bmatrix} 1 \\ 2 \end{bmatrix} + \cos\left(\frac{5\sqrt{6}}{3}t\right) \begin{bmatrix} 0 \\ \sqrt{6} \end{bmatrix} \right\}$$

Initial Condition:

$$\begin{bmatrix} I_1(0) \\ I_2(0) \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \end{bmatrix} \xrightarrow{\textcolor{red}{\Rightarrow}} \begin{bmatrix} 0 \\ 0 \end{bmatrix} = \begin{bmatrix} 2 \\ 0 \end{bmatrix} + C_1 \begin{bmatrix} 1 \\ 2 \end{bmatrix} + C_2 \begin{bmatrix} 0 \\ \sqrt{6} \end{bmatrix} \xrightarrow{\textcolor{red}{\Rightarrow}} \begin{bmatrix} C_1 \\ C_2 \end{bmatrix} = \begin{bmatrix} -2 \\ \frac{2}{3}\sqrt{6} \end{bmatrix}$$

Solution of the initial value problem:

$$I_1(t) = 2 - 2e^{-5t} \cos\left(\frac{5\sqrt{6}}{3}t\right) + \frac{2}{3}\sqrt{6}e^{-5t} \sin\left(\frac{5\sqrt{6}}{3}t\right)$$

$$I_2(t) = \frac{10}{3}\sqrt{6}e^{-5t} \sin\left(\frac{5\sqrt{6}}{3}t\right)$$

$$I_3(t) = I_1(t) + I_2(t) = 2 - 2e^{-5t} \cos\left(\frac{5\sqrt{6}}{3}t\right) + 4\sqrt{6}e^{-5t} \sin\left(\frac{5\sqrt{6}}{3}t\right)$$

Example 2. (continued. Figures.)

General solutions:


$$\begin{bmatrix} I_1(t) \\ I_2(t) \end{bmatrix} = \begin{bmatrix} 2 \\ 0 \end{bmatrix} + C_1 e^{-5t} \left\{ \cos\left(\frac{5\sqrt{6}}{3}t\right) \begin{bmatrix} 1 \\ 2 \end{bmatrix} - \sin\left(\frac{5\sqrt{6}}{3}t\right) \begin{bmatrix} 0 \\ \sqrt{6} \end{bmatrix} \right\} \\ + C_2 e^{-5t} \left\{ \sin\left(\frac{5\sqrt{6}}{3}t\right) \begin{bmatrix} 1 \\ 2 \end{bmatrix} + \cos\left(\frac{5\sqrt{6}}{3}t\right) \begin{bmatrix} 0 \\ \sqrt{6} \end{bmatrix} \right\}$$

Example 2. (continued. Figures.)

General solutions:

$$\begin{bmatrix} I_1(t) \\ I_2(t) \end{bmatrix} = \begin{bmatrix} 2 \\ 0 \end{bmatrix} + C_1 e^{-5t} \left\{ \cos\left(\frac{5\sqrt{6}}{3}t\right) \begin{bmatrix} 1 \\ 2 \end{bmatrix} - \sin\left(\frac{5\sqrt{6}}{3}t\right) \begin{bmatrix} 0 \\ \sqrt{6} \end{bmatrix} \right\}$$
$$+ C_2 e^{-5t} \left\{ \sin\left(\frac{5\sqrt{6}}{3}t\right) \begin{bmatrix} 1 \\ 2 \end{bmatrix} + \cos\left(\frac{5\sqrt{6}}{3}t\right) \begin{bmatrix} 0 \\ \sqrt{6} \end{bmatrix} \right\}$$

The Graphs of Currents vs Time

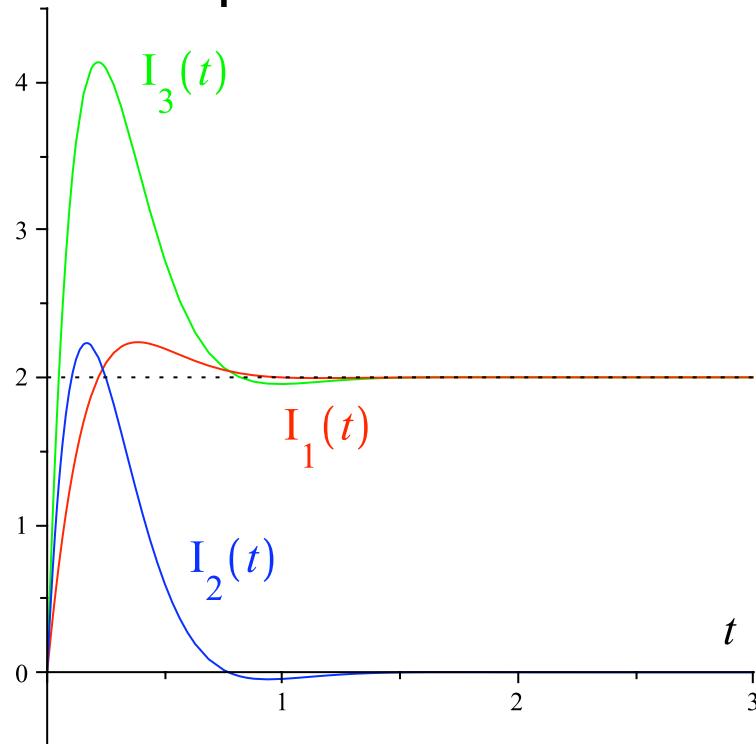


Example 2. (continued. Figures.)

General solutions:

$$\begin{bmatrix} I_1(t) \\ I_2(t) \end{bmatrix} = \begin{bmatrix} 2 \\ 0 \end{bmatrix} + C_1 e^{-5t} \left\{ \cos\left(\frac{5\sqrt{6}}{3}t\right) \begin{bmatrix} 1 \\ 2 \end{bmatrix} - \sin\left(\frac{5\sqrt{6}}{3}t\right) \begin{bmatrix} 0 \\ \sqrt{6} \end{bmatrix} \right\} + C_2 e^{-5t} \left\{ \sin\left(\frac{5\sqrt{6}}{3}t\right) \begin{bmatrix} 1 \\ 2 \end{bmatrix} + \cos\left(\frac{5\sqrt{6}}{3}t\right) \begin{bmatrix} 0 \\ \sqrt{6} \end{bmatrix} \right\}$$

The Graphs of Currents vs Time

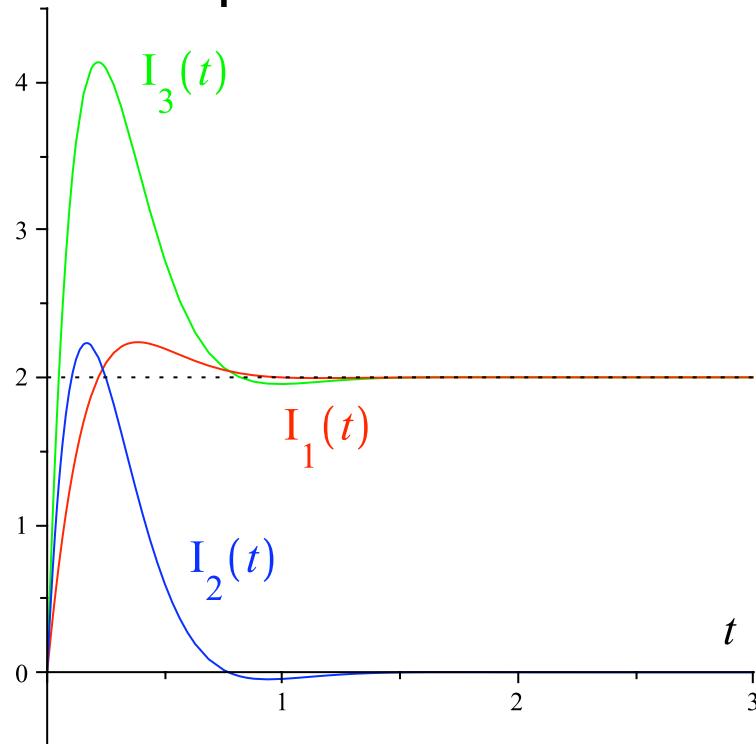

Phase Portrait.
Equilibrium (2,0) is an Attractive Focus

