

Electric Circuits
& Diff Eqs of 2nd order

- Faraday's Law



L : inductance
 i : electric current

$$(\text{voltage drop across the inductor}) = L \frac{di}{dt}$$


- Ohm's Law



R : resistance
 i : electric current

$$(\text{voltage drop across the resistor}) = Ri$$

- Coulomb's Law

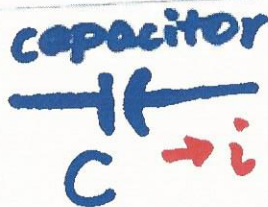

C : capacitance
 Q : electric charge on capacitor

$$(\text{voltage drop across the capacitor}) = \frac{Q}{C}$$

- electric current $i = \frac{dQ}{dt}$

- Kirchhoff's voltage Law

$$(\text{the sum of voltage drops in any loop}) = 0$$

LC Circuit


L : inductor

C : capacitor

i : electric current

Q : electric charge on the capacitor

v : voltage drop across the capacitor

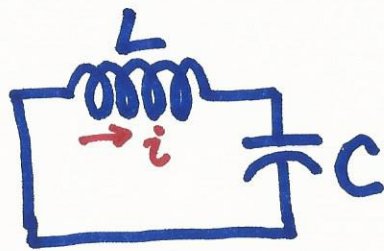

$$(*) \quad L \frac{di}{dt} + \frac{Q}{C} = 0$$

$$\begin{cases} i = \frac{dQ}{dt} \\ v = \frac{Q}{C} \end{cases} \Rightarrow i = C \frac{dv}{dt}$$

A 2nd order Diff Eq for Q

$$L \frac{d^2 Q}{dt^2} + \frac{1}{C} Q = 0$$

A 2nd order Diff Eq for i

$$L \frac{d^2 i}{dt^2} + \frac{1}{C} i = 0$$

A 2nd order Diff Eq for v

$$LC \frac{d^2 v}{dt^2} + v = 0$$

LC Circuit


L : inductor

C : capacitor

i : electric current

Q : electric charge on the capacitor

v : voltage drop across the capacitor

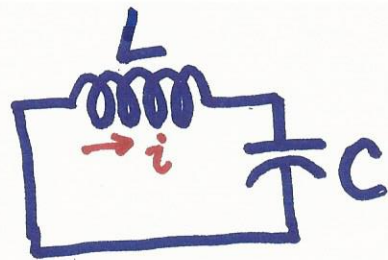

$$(*) \quad L \frac{di}{dt} + \frac{Q}{C} = 0$$

$$\begin{cases} i = \frac{dQ}{dt} \\ v = \frac{Q}{C} \end{cases} \Rightarrow i = C \frac{dv}{dt}$$

A System of Diff Eq's for Q and i

$$\begin{cases} \frac{dQ}{dt} = i \\ \frac{di}{dt} = -\frac{1}{LC} Q \end{cases}$$


$$\frac{d}{dt} \begin{bmatrix} Q \\ i \end{bmatrix} = \begin{bmatrix} 0 & 1 \\ -\frac{1}{LC} & 0 \end{bmatrix} \begin{bmatrix} Q \\ i \end{bmatrix}$$

A System of Diff Eq's for v and i

$$\begin{cases} \frac{dv}{dt} = \frac{1}{C} i \\ \frac{di}{dt} = -\frac{1}{L} v \end{cases}$$

$$\frac{d}{dt} \begin{bmatrix} v \\ i \end{bmatrix} = \begin{bmatrix} 0 & \frac{1}{C} \\ -\frac{1}{L} & 0 \end{bmatrix} \begin{bmatrix} v \\ i \end{bmatrix}$$

RLC circuit

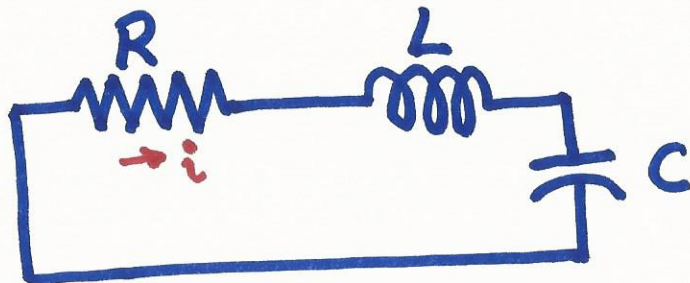

$$(*) \quad Ri + L \frac{di}{dt} + \frac{Q}{C} = 0$$

$$\begin{cases} i = \frac{dQ}{dt} \\ v = \frac{Q}{C} \end{cases} \Rightarrow i = C \frac{dv}{dt}$$

Diff Eq for Q (electric charge on the capacitor)

$$L \frac{d^2 Q}{dt^2} + R \frac{dQ}{dt} + \frac{1}{C} Q = 0$$


Diff Eq for i (electric current)

$$L \frac{d^2 i}{dt^2} + R \frac{di}{dt} + \frac{1}{C} i = 0$$

Diff Eq for v (voltage drop across the capacitor)

$$LC \frac{d^2 v}{dt^2} + RC \frac{dv}{dt} + v = 0$$

RLC Circuit

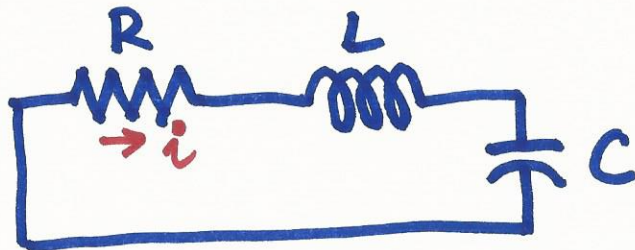

$$(*) \quad Ri + L \frac{di}{dt} + \frac{Q}{C} = 0$$

$$\begin{cases} i = \frac{dQ}{dt} \\ V = \frac{Q}{C} \end{cases} \Rightarrow i = C \frac{dV}{dt}$$

A system of Diff Eqs for $\begin{cases} Q \\ i \end{cases}$ (electric charge on the capacitor)
(electric current)

$$\begin{cases} \frac{dQ}{dt} = i \\ \frac{di}{dt} = -\frac{1}{LC}Q - \frac{R}{L}i \end{cases}$$


$$\frac{d}{dt} \begin{bmatrix} Q \\ i \end{bmatrix} = \begin{bmatrix} 0 & 1 \\ -\frac{1}{LC} & -\frac{R}{L} \end{bmatrix} \begin{bmatrix} Q \\ i \end{bmatrix}$$

A system of Diff Eqs for $\begin{cases} V \\ i \end{cases}$ (voltage drop across the capacitor)
(electric current)

$$\begin{cases} \frac{dV}{dt} = \frac{1}{C}i \\ \frac{di}{dt} = -\frac{1}{L}V - \frac{R}{L}i \end{cases}$$

$$\frac{d}{dt} \begin{bmatrix} V \\ i \end{bmatrix} = \begin{bmatrix} 0 & \frac{1}{C} \\ -\frac{1}{L} & -\frac{R}{L} \end{bmatrix} \begin{bmatrix} V \\ i \end{bmatrix}$$

RLC Circuit

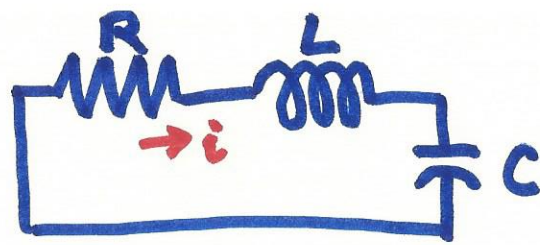


- 2nd Order Diff Eq for i (electric current): $L \frac{d^2 i}{dt^2} + R \frac{di}{dt} + \frac{1}{C} i = 0$

- Characteristic Polynomial and Eigenvalues:

$$L\lambda^2 + R\lambda + \frac{1}{C} = 0. \quad \lambda = \frac{-R \pm \sqrt{R^2 - 4L/C}}{2L}$$


Un-Damped Circuit

$R=0$ i.e. LC circuit

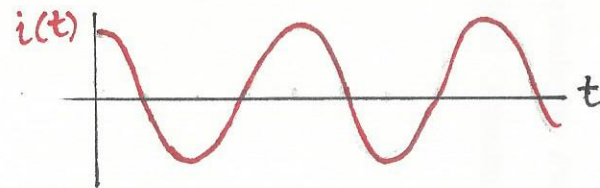


Under-Damped Circuit

$$R > 0, R^2 - 4\frac{L}{C} < 0$$

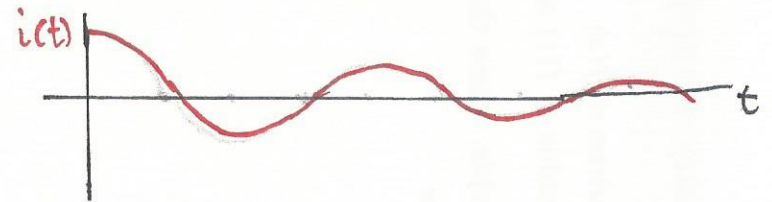

Critically-Damped Circuit
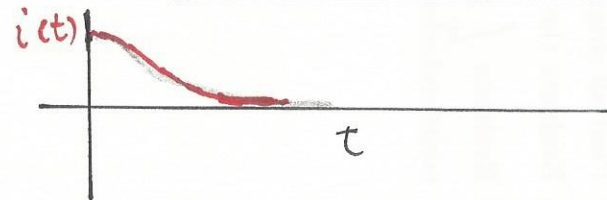
$$R^2 - 4\frac{L}{C} = 0, \text{ i.e. } R = 2\sqrt{\frac{L}{C}}$$




Over-Damped Circuit

$$R > 0, R^2 - 4\frac{L}{C} > 0$$



RLC Circuit

with Voltage Source

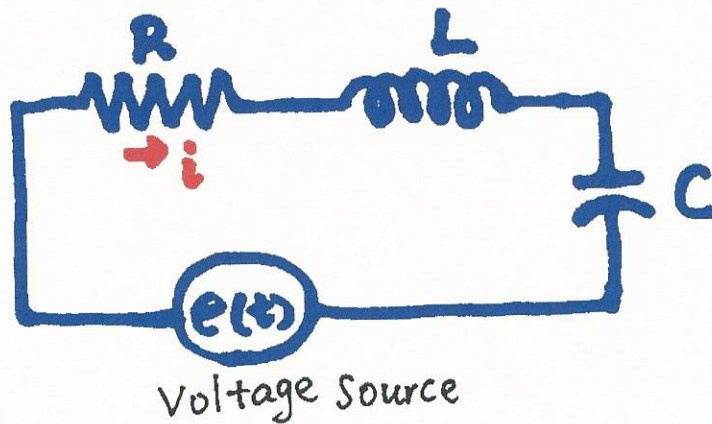

$$(*) \quad Ri + L \frac{di}{dt} + \frac{Q}{C} - e(t) = 0$$

$$i = \frac{dQ}{dt}$$
$$v = \frac{Q}{C}$$

Diff Eq for Q (electric charge on the capacitor)

$$L \frac{d^2 Q}{dt^2} + R \frac{dQ}{dt} + \frac{Q}{C} = e(t)$$

Nonhomogeneous Linear Diff Eq

Diff Eq for i (Current)

$$L \frac{d^2 i}{dt^2} + R \frac{di}{dt} + \frac{1}{C} i = e(t)$$

Diff Eq for v (voltage drop across the capacitor)

$$LC \frac{d^2 v}{dt^2} + RC \frac{dv}{dt} + v = e(t)$$